



North South University
Department of Electrical & Computer Engineering

ASSIGNMENT

Course Name: Digital Logic Design

Course Code: CSE231

Section: 01

Assignment Name: Constructing a Sequential Circuit using JK, D and T Flip-Flops

Submitted To: Taoseef Ishtiaq

Assignment Date: 20/09/2020

Submission Date: 23/09/2020

Student Name:	Student ID:	Score
Md Sazid Ahmed Tonmoy	1911498642	
Remarks:		

Sequential Diagram:

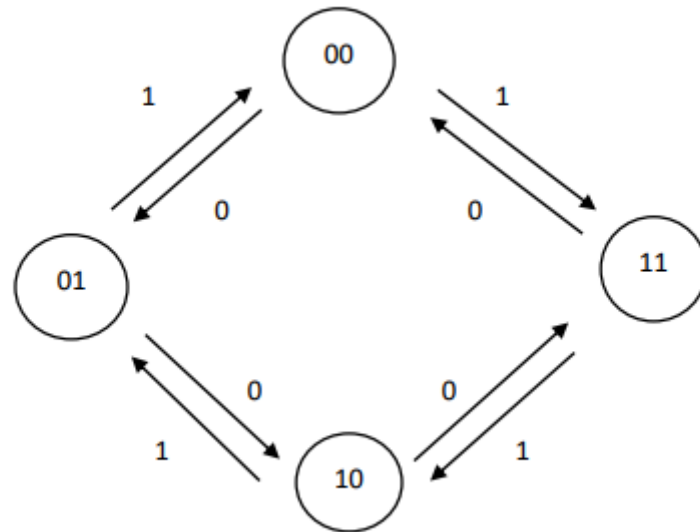


Figure: State Diagram for a Synchronous Sequential Circuit

The Number of inputs in the Diagram = 1(X)

The Number of state variable in the Diagram = 2 (A, B)

When we give input $x = 0$ loop will go anti-clock wise.

When we give input $x = 1$, loop will go clock wise.

Constructing a Sequential Circuit using D Flip-Flops:

Previous State		Inputs	Next State		Flip-Flop Input Function	
A	B	X	A	B	D _A	D _B
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0

K-maps:

A\BX	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D_A = AB'X' + A'B'X + A'BX' + ABX$$

A\BX	00	01	11	10
0	1	1	0	0
1	1	1	0	0

$$D_B = B'$$

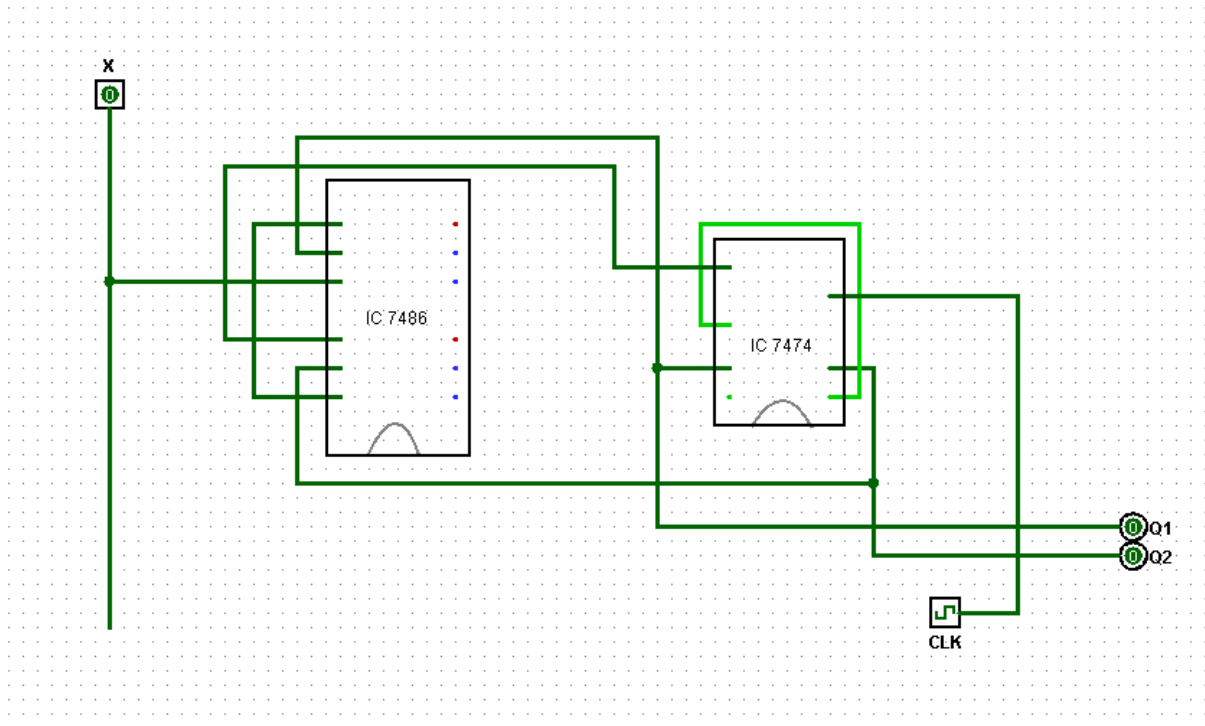


Figure: Sequential Circuit using D Flip-Flops

Constructing a Sequential Circuit using T Flip-Flops:

Previous State		Inputs	Next State		Flip-Flop Input Function	
A	B	X	A	B	T _A	T _B
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	1
0	1	1	0	0	0	1
1	0	0	1	1	0	1
1	0	1	0	1	1	1
1	1	0	0	0	1	1
1	1	1	1	0	0	1

K-maps:

A\BX	00	01	11	10
0	0	1	0	1
1	0	1	0	1

$$T_A = B'X + BX'$$

A\BX	00	01	11	10
0	1	1	1	1
1	1	1	1	1

$$T_B = 1$$

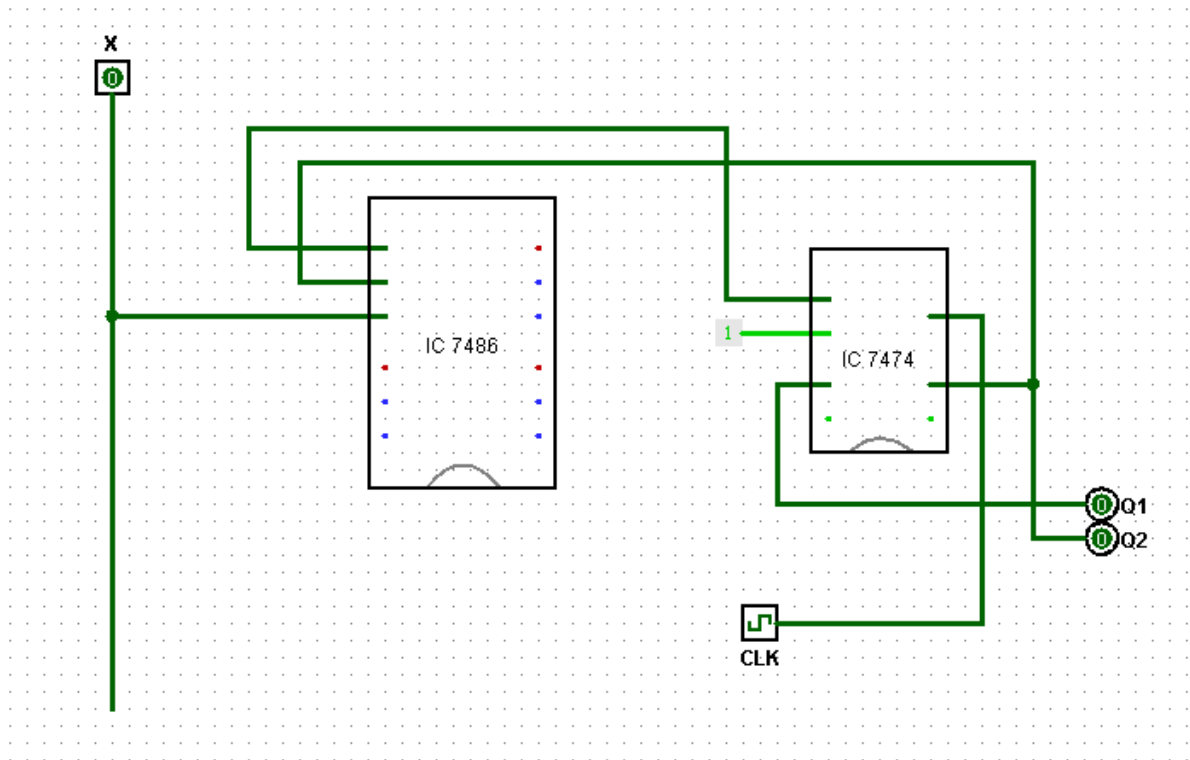


Figure: Sequential Circuit using T Flip-Flops

Constructing a Sequential Circuit using JK Flip-Flops:

Previous State		Inputs	Next State		Flip-Flop Input Function			
A	B	X	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	X	1	X
0	0	1	1	1	1	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	0	0	X	X	1
1	0	0	1	1	X	0	1	X
1	0	1	0	1	X	1	1	X
1	1	0	0	0	X	1	X	1
1	1	1	1	0	X	0	X	1

K-Maps:

A\BX	00	01	11	10
0	0	1	0	1
1	X	X	X	X

$$J_A = B'X + BX'$$

A\BX	00	01	11	10
0	X	X	X	X
1	0	1	0	1

$$K_A = B'X + BX'$$

A\BX	00	01	11	10
0	1	1	X	X
1	1	1	X	X

$$J_B = 1$$

A\BX	00	01	11	10
0	X	X	1	1
1	X	X	1	1

$$K_B = 1$$

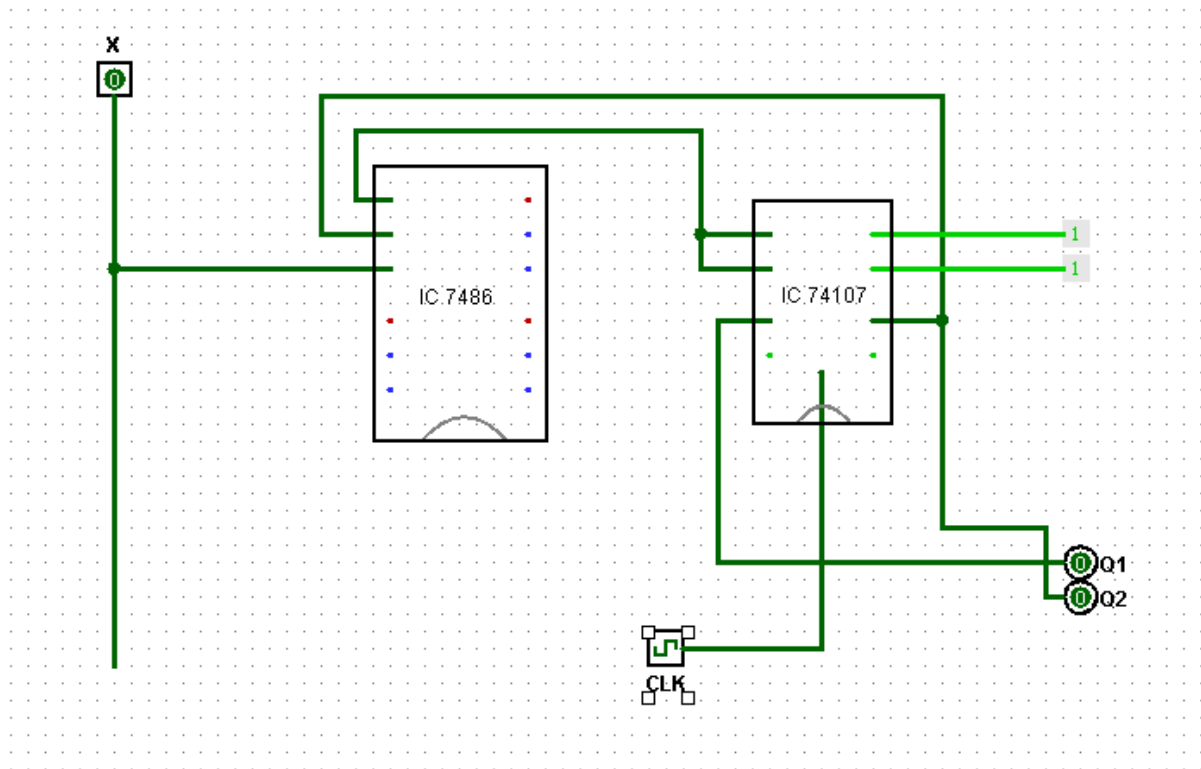


Figure: Sequential Circuit using JK Flip-Flops